

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
SEVENTH SEMESTER B.TECH DEGREE EXAMINATION(S), MAY 2019

**Course Code: EC461**

**Course Name: MICROWAVE DEVICES AND CIRCUITS**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer any two full questions, each carries 15 marks.*

Marks

- |   |   |      |
|---|---|------|
| 1 | a) What are the limitations of conventional solid state devices at microwave?   | (5)  |
|   | b) Explain modes of operation of Gunn diode   | (7)  |
|   | c) State Gunn effect.   | (3)  |
| 2 | a) Design a one port negative resistance oscillator.  | (5)  |
|   | b) Design a single stage Transistor Amplifier used in microwave circuits  | (10) |
| 3 | a) What is MESFET ? Mention its structure and operation.  | (10) |
|   | b) An IMPATT diode has carrier drift velocity $V_d = 3 \times 10^7$ cm/s, Drift region length $L = 6\mu\text{m}$ , Maximum operating voltage $V_{0\text{max}} = 100\text{V}$ , Maximum operating current $I_{0\text{max}} = 200\text{mA}$ , Efficiency $\eta = 15\%$ , Breakdown voltage $V_{\text{bd}} = 90\text{V}$ . Find maximum CW output power in watts and the resonant frequency in gigahertz | (5)  |

**PART B**

*Answer any two full questions, each carries 15 marks.*

- |   |   |      |
|---|---|------|
| 4 | a) For a microwave circuit , discuss the equivalent voltage and currents .  | (10) |
|   | b) Derive expressions for S parameters in terms of Z parameters for a 2-port network.   | (5)  |
| 5 | a) Explain the principle of double stub matching  | (5)  |
|   | b) What are the steps required to transfer a LPF from HPF .explain.   | (10) |
| 6 | a) List the Kuroda's identity.  | (5)  |
|   | b) Design a low-pass composite filter with a cut-off frequency of 2MHz and impedances of $75\Omega$ . Place the infinite attenuation pole at 2.05MHz. | (10) |

**PART C**

*Answer any two full questions, each carries 20 marks.*

- |   |   |      |
|---|---|------|
| 7 | a) Analyse the hybrid MMICs   | ( 8) |
|   | b) Discuss Stripline in planar transmission and also find the Quality factor. | ( 8) |
|   | c) What is Monolithic MICs and Discuss its construction.                      | (4)  |

- 8 a) What are limiters? Explain different types of limiters (8)
- b) Explain the working and applications of Circulators and Isolators. (8)
- c) Explain the working of diode switches and attenuators? (4)
- 9 a) Explain the configuration of Planar capacitor film (5)
- b) Discuss Microwave resonators with neat diagram (8)
- c) Classify the losses in Microstrip lines (7)

\*\*\*\*