

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**FOURTH SEMESTER B.TECH DEGREE EXAMINATION(R&S), MAY 2019**

**Course Code: EC212**

**Course Name: LINEAR INTEGRATED CIRCUITS AND DIGITAL ELECTRONICS  
(MC)**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions, each carries 5 marks.*

- |   | Marks |
|---|-------|
| 1 List and explain the characteristics of Op-Amp.   | (5)   |
| 2 Differentiate between PAL and PLA.  | (5)   |
| 3 Comment on clippers and clampers using Op-Amp IC.   | (5)   |
| 4 Using Boolean algebra, verify $AB + \overline{A}C + BC = AB + \overline{A}C$  | (5)   |
| 5 Obtain an expression for first order low pass filter (LPF).   | (5)   |
| 6 Draw the logic diagram of a master- slave J-K flip-flop using NAND gates and Explain how the race around condition is eliminated in it. | (5)   |
| 7 Distinguish between half adder and full adder. Give the truth table and logic circuit of half adder and full adder.                     | (5)   |
| 8 Design a 4 bit ring counter using JK flip flop and also draw its output waveform.   | (5)   |

**PART B**

*Answer any three full questions, each carries 10 marks.*

- |  |      |
|--|------|
| 9 Elucidate in detail the working of a monostable and astable multivibrator using Op-Amp IC 741. | (10) |
| 10 a) Explain how an Op-Amp works as a differentiator.   | (5)  |
| b) Interpret the following   | (5)  |
| i) V-I converter with floating load  |      |
| ii) V-I converter with ground load   |      |
| 11 a) How a 4 bit R-2R ladder DAC works?   | (5)  |
| b) Define A/D converter and explain any one of its type.   | (5)  |
| 12 Draw the circuit of a Log and Antilog amplifier using Op-Amp and derive its output voltage.   | (10) |
| 13 Minimize the following using K-map  |      |
| a) $F(A,B,C,D) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$                                    | (10) |
| b) $F(P,Q,R,S) = \pi (3, 5, 7, 8, 10, 11, 12, 13)$   |      |

**PART C**

*Answer any two full questions, each carries 15 marks.*

- 14 a) Implement the following Boolean function  $F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 10, 11, 14, 15)$  by using 8X1 multiplexer. (9)
- b) What is a multiplexer? Draw a logic diagram and logic symbol of a 4 to 1 MUX with the help of truth table. (6)
- 15 Design and implement a 4 bit synchronous up counter by using JK flip flops. (15)
- 16 a) Design and implement a 4 bit binary to gray code converter. (10)
- b) Design and implement a 3-to-8 decoder. (5)
- 17 a) Design a sequence detector that produces an output '1' whenever the non overlapping sequence 1011 is detected (10)
- b) Draw a 4 bit binary asynchronous up counter. (5)

\*\*\*\*